

# Op amp linearizes attenuator control response

Mike Irwin, Shawville, PQ, Canada


**P**ROFESSIONAL-AUDIO equipment commonly uses Analog Devices' (www.analog.com)

high-performance, quad-voltage-controlled SSM2164 attenuator. The control response is  $-30 \text{ dB/V}$ , with  $0\text{V}$  producing unity gain. Attenuation increases as the applied control voltage increases in the positive direction. The circuit in **Figure 1** extends the range of applications for this versatile chip by providing a simple means of linearizing the control response. The result is an amplifier with gain directly proportional to the control voltage. In addition, the circuit also functions as a simple logarithm generator. You can use a single SSM2164 to make two high-quality, linear voltage-controlled amplifiers using this method. The four gain cells in the SSM2164 are tightly matched, current-in, current-out transconductance multipliers. The control response of each gain cell is:  $\text{gain} = 10^{(-V/0.67)}$ . The cells are noninverting structures.

(matching) "slave" cell, which processes the audio signal. Op amp  $IC_1$  maintains its inverting input at virtual ground by servo-controlling the gain of the master SSM2164 cell, which connects to the negative reference voltage. The output of  $IC_1$  is a logarithmic function of the input:  $V_{OUT} = -0.67 \log[(-V_{IN}R_2)/(V_{REF}R_1)]$ .  $V_{IN}$  is the gain-control voltage, and  $V_{REF}$  is the negative reference voltage.  $V_{OUT}$  then drives the control pin of the slave cell. Substituting the expression for  $V_{OUT}$  for  $V$  in the expression for gain yields the following:  $\text{gain} = (V_{IN}R_2)/(V_{REF}R_1)$ , which is the desired linear response.

Op amp  $IC_2$  converts the slave cell's output current to an audio voltage with a gain of  $R_4/R_3$ . The overall expression for the gain is:  $\text{gain} = (V_{IN}R_2R_4)/(V_{REF}R_1R_3)$ . If  $R_1 = R_2$  and  $R_3 = R_4$ , the expression reduces to:  $\text{gain} = V_{IN}/V_{REF}$ , and gain (in decibels)  $= 20 \log(V_{IN}/V_{REF})$ . Setting  $V_{IN}$  to  $15\text{V}$  and  $V_{REF}$  to  $-15\text{V}$  produces unity

**Figure 1**

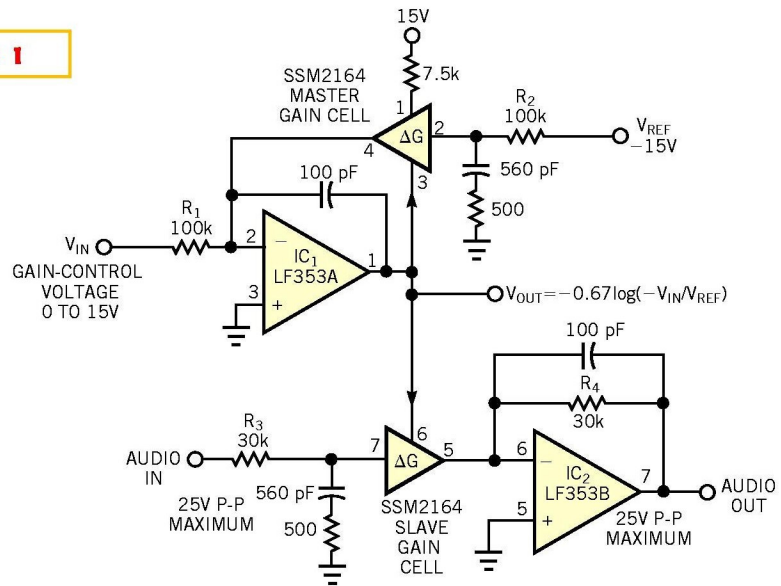

You can obtain both a gain-controlled output and a logarithmic output using this configuration.


Each voltage-controlled amplifier uses two gain cells. A "master" cell in the feedback loop of an op amp generates a log-

arithmic voltage output in response to a linear voltage input. This log voltage then goes to the control pin of the second

0 to  $15\text{V}$  range. The circuit produces no audible clicks and works well at lower supply voltages, such as  $\pm 5\text{V}$ .

For best performance,  $IC_1$  should be a low-offset, low-input-current unit, and  $IC_2$  should be a high-quality, low-noise audio op amp. However, you can obtain reasonably good performance with inexpensive op amps, such as the TL072 and LF353. The prototype unit achieved a control range of 75 to 80 dB, using an OP-290 for  $IC_1$ . The control-voltage feedthrough on the audio output is minimal, varying 10 to 20 mV when you sweep the gain through a 70-dB range. The noise and distortion performance is excellent, because the design uses the gain cells in the standard configuration in the SSM2164 data sheet.

**Figure 2**

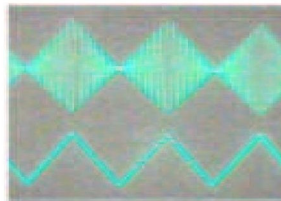

The lower trace is a 0 to 3V triangle wave, which you use to modulate the 10-kHz sine wave in the upper trace. Note the linear modulation envelope.

gain with the indicated component values. The gain decreases smoothly to  $-70$  to  $-80 \text{ dB}$  as the control voltage decreases (**Figure 2**). The voltage-controlled amplifier then shuts off completely (attenuation = 100 dB) when the control voltage drops to within a few millivolts of  $0\text{V}$ . Negative voltages make the output of  $IC_1$  swing close to the positive rail, but  $IC_1$  promptly comes off the rail when the control voltage returns to the

**Is this the best Design Idea in this issue?** Select at [www.edn.com](http://www.edn.com).